



INDIAN INSTITUTE OF SCIENCE, BENGALURU

DEPARTMENT OF ELECTRONIC SYSTEMS
ENGINEERING

DESIGN FOR ANALOG CIRCUITS
LABORATORY REPORT

ASSIGNMENT 8
ACTIVE SECOND ORDER FILTERS

SOUMYA KANTA RANA
S.R. No. : 04-01-00-10-51-21-1-19261

October 2, 2021

Contents

1	KRC Low Pass Filter	1
1.1	Aim	1
1.2	Schematic	1
1.3	Component Selection	1
1.4	Frequency Response	1
1.5	Transient Response	2
2	KRC High Pass Filter	3
2.1	Aim	3
2.2	Schematic	3
2.3	Component Selection	3
2.4	Frequency Response	3
2.5	Transient Response	4
3	Twin-T Notch Filter	5
3.1	Aim	5
3.2	Schematic	5
3.3	Component Selection	5
3.4	Frequency Response	5
3.5	Transient Response	6
4	Multiple-feedback Band Pass Filter	7
4.1	Aim	7
4.2	Schematic	7
4.3	Component Selection	7
4.4	Frequency Response	7
4.5	Transient Response	8
5	Conclusion	8

List of Figures

1	LTSpice schematic of KRC low pass filter	1
2	Frequency response of KRC low pass filter	1
3	Transient response of KRC low pass filter	2
4	LTSpice schematic of KRC high pass filter	3
5	Frequency response of KRC high pass filter	3
6	Transient response of KRC high pass filter	4
7	LTSpice schematic of Twin-T notch filter	5
8	Frequency response of Twin-T notch filter	5
9	Transient response of Twin-T notch filter	6
10	LTSpice schematic of multiple-feedback bandpass filter	7
11	Frequency response of multiple-feedback bandpass filter	7
12	Transient response of multiple-feedback bandpass filter	8

1 KRC Low Pass Filter

1.1 Aim

To perform transient and frequency domain simulations of KRC low pass filter.

1.2 Schematic

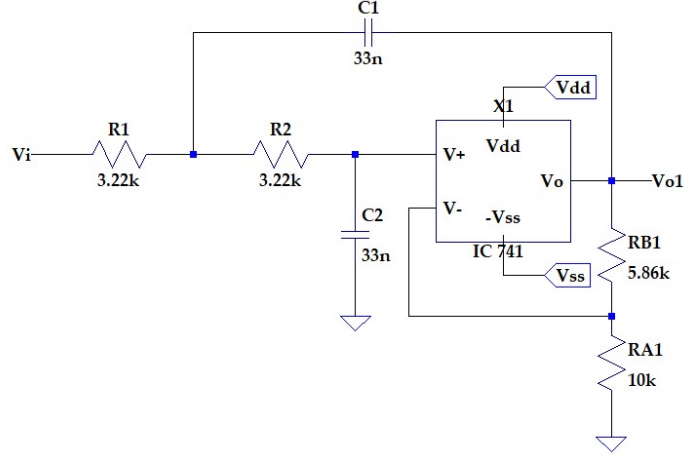


Figure 1: LTSpice schematic of KRC low pass filter

1.3 Component Selection

The transfer function of the filter is given by

$$\frac{V_{o1}(s)}{V_i(s)} = \frac{K}{s^2 R_1 C_1 R_2 C_2 + s(C_2 R_2 + C_2 R_1 + (1 - K)C_1 R_1) + 1} \quad (1)$$

Where $K = 1 + R_{B1}/R_{A1}$. Choosing $C_1 = C_2$, $R_1 = R_2$, we have

$$H_{LP} = K, \omega_0 = \frac{1}{R_1 C_1}, Q = \frac{1}{3 - K}$$

For obtaining $\omega_0 = 2\pi \times 1.5 \text{krad/s}$ and $Q = 0.707$, the values chosen are $R_1 = R_2 = 3.22 \text{k}\Omega$, $C_1 = C_2 = 33 \text{nF}$, $R_{A1} = 5.86 \text{k}\Omega$, $R_{B1} = 10 \text{k}\Omega$.

1.4 Frequency Response

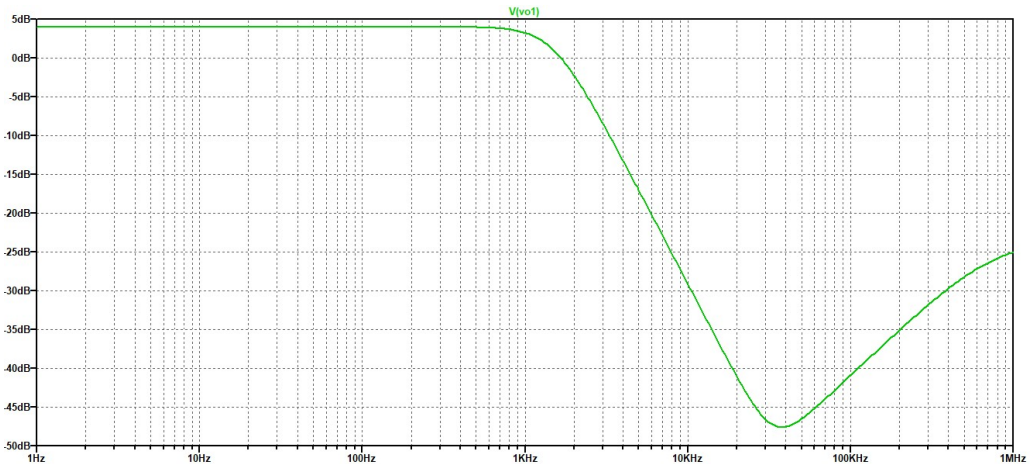


Figure 2: Frequency response of KRC low pass filter

The figure 2 above shows the frequency response of the KRC low pass filter. The cutoff frequency obtained is 1.498 kHz.

1.5 Transient Response

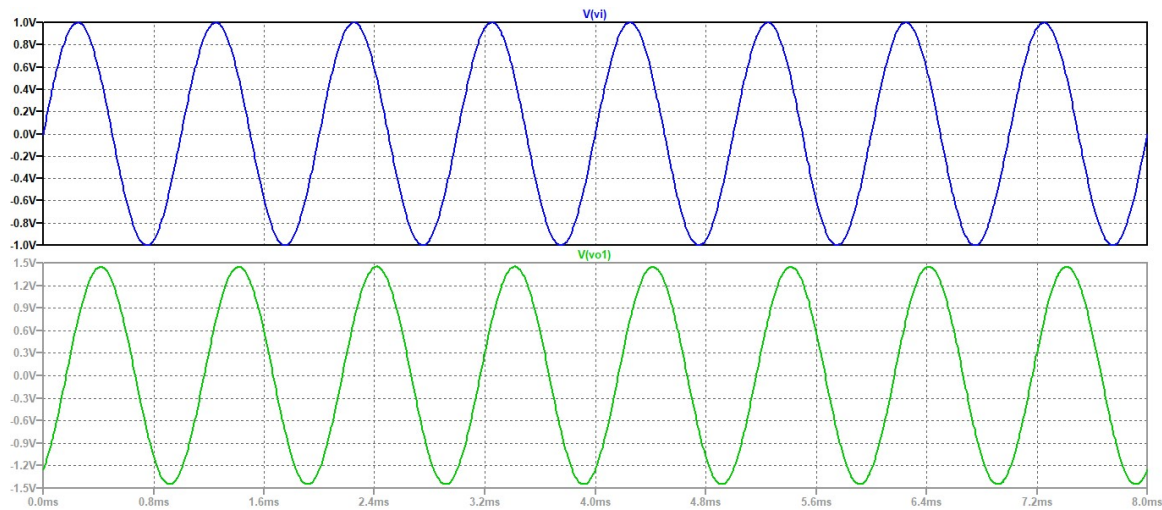


Figure 3: Transient response of KRC low pass filter

The figure 3 above shows the transient response of the KRC low pass filter with 1 V, 1 kHz sinewave input. The output voltage amplitude obtained is 1.45 V.

2 KRC High Pass Filter

2.1 Aim

To perform transient and frequency domain simulations of KRC high pass filter.

2.2 Schematic

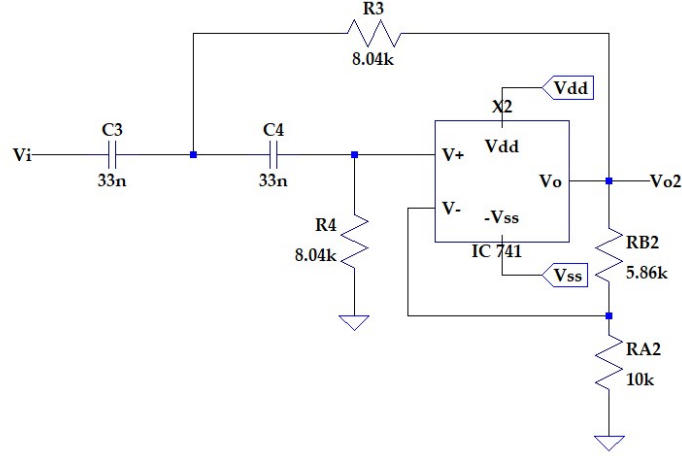


Figure 4: LTSpice schematic of KRC high pass filter

2.3 Component Selection

The transfer function of the filter is given by

$$\frac{V_{o2}(s)}{V_i(s)} = \frac{K s^2}{s^2 R_3 C_3 R_4 C_4 + s(C_4 R_4 + C_4 R_3 + (1 - K)C_3 R_3) + 1} \quad (2)$$

Where $K = 1 + R_{B2}/R_{A2}$. Choosing $C_3 = C_4$, $R_3 = R_4$, we have

$$H_{HP} = K, \omega_0 = \frac{1}{R_3 C_3}, Q = \frac{1}{3 - K}$$

For obtaining $\omega_0 = 2\pi \times 0.6 \text{krad/s}$ and $Q = 0.707$, the values chosen are $R_3 = R_4 = 8.04 \text{k}\Omega$, $C_3 = C_4 = 33 \text{nF}$, $R_{B2} = 5.86 \text{k}\Omega$, $R_{A2} = 10 \text{k}\Omega$.

2.4 Frequency Response

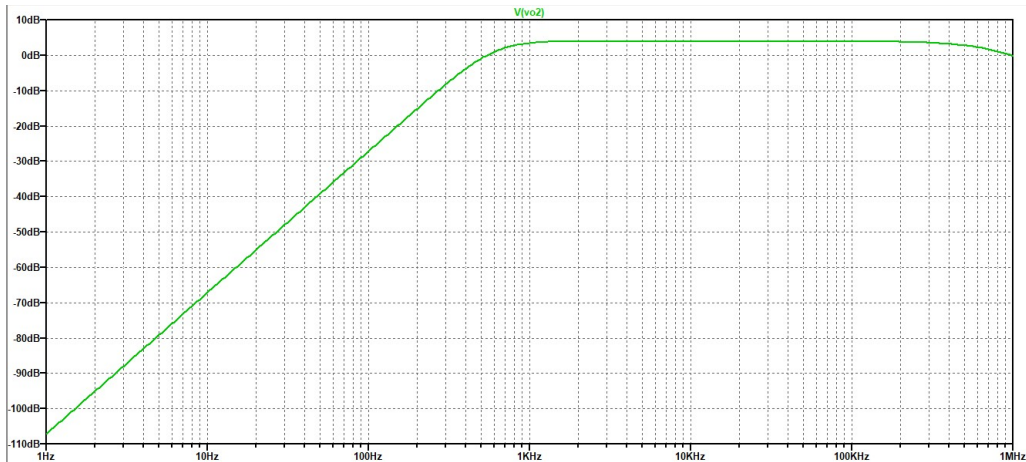


Figure 5: Frequency response of KRC high pass filter

The figure 5 above shows the frequency response of the KRC high pass filter. The cutoff frequency obtained is 599.7 Hz.

2.5 Transient Response

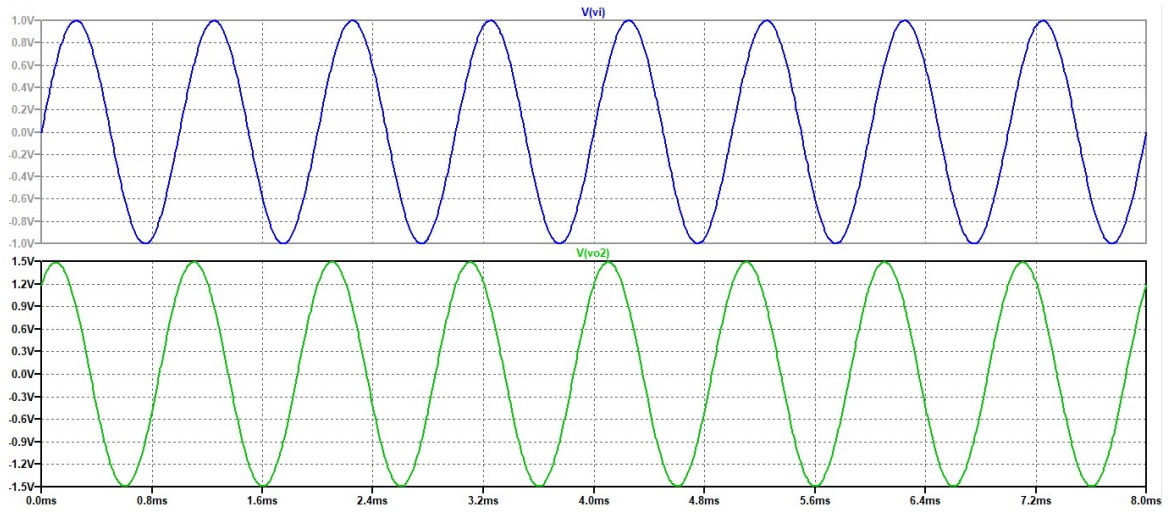


Figure 6: Transient response of KRC high pass filter

The figure 6 above shows the transient response of the KRC high pass filter with 1 V, 1 kHz sinewave input. The output voltage amplitude obtained is 1.49 V.

3 Twin-T Notch Filter

3.1 Aim

To perform transient and frequency domain simulations of Twin-T Notch filter.

3.2 Schematic

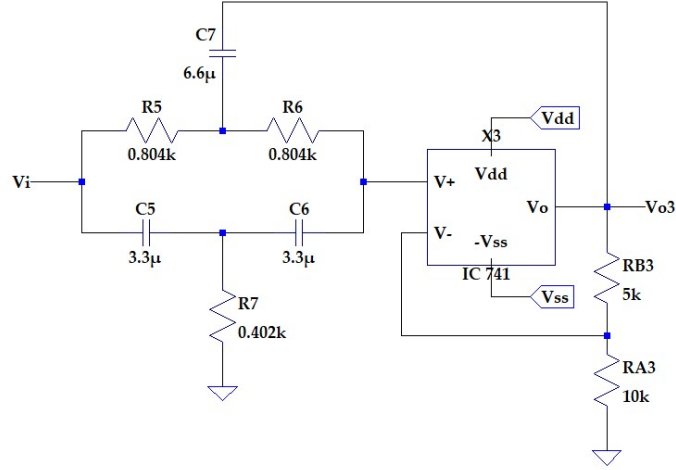


Figure 7: LTSpice schematic of Twin-T notch filter

3.3 Component Selection

Choosing $R_5 = R_6 = 2R_7$, $C_5 = C_6 = C_7/2$, the transfer function of the filter is given by

$$\frac{V_{o3}(s)}{V_i(s)} = K \frac{(1 + s^2 R_5^2 C_5^2)}{s^2 R_5^2 C_5^2 + s(4 - 2K)R_5 C_5 + 1} \quad (3)$$

Where $K = 1 + R_{B3}/R_{A3}$. The parameters of the filter are

$$H_{0N} = K, \omega_0 = \frac{1}{R_5 C_5}, Q = \frac{1}{4 - 2K}$$

For obtaining $\omega_0 = 2\pi \times 60 \text{ rad/s}$ the values chosen are $C_5 = C_6 = C_7/2 = 3.3\mu\text{F}$, $R_5 = R_6 = 2R_7 = 0.804\text{k}\Omega$ and $K = 1.5$ ($R_{B3} = 5\text{k}\Omega$, $R_{A3} = 10\text{k}\Omega$).

3.4 Frequency Response

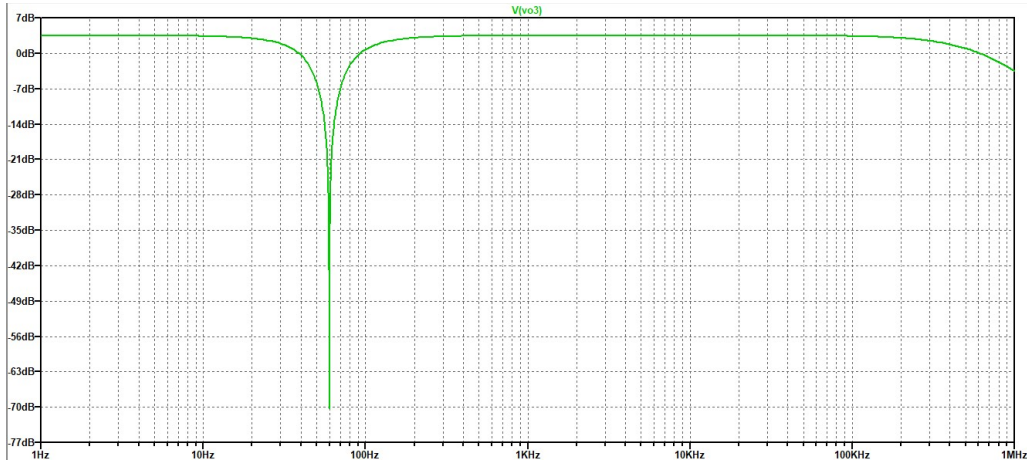


Figure 8: Frequency response of Twin-T notch filter

The figure 8 above shows the frequency response of the Twin-T notch filter. The notch frequency obtained is 59.98 Hz.

3.5 Transient Response

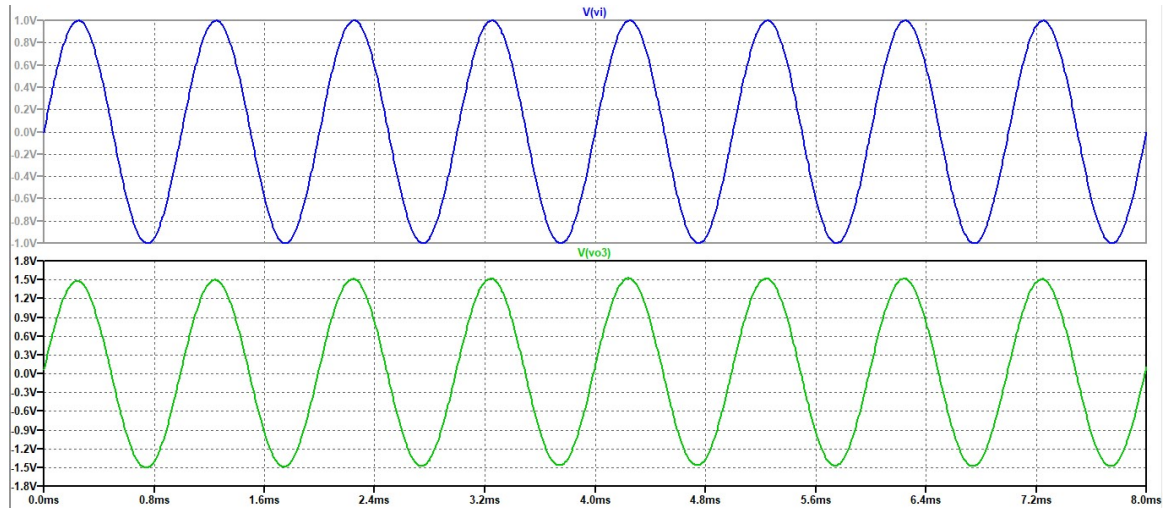


Figure 9: Transient response of Twin-T notch filter

The figure 9 above shows the transient response of the Twin-T notch filter with 1 V, 1 kHz sinewave input. The output voltage amplitude obtained is 1.50 V.

4 Multiple-feedback Band Pass Filter

4.1 Aim

To perform transient and frequency domain simulations of multiple-feedback bandpass filter.

4.2 Schematic

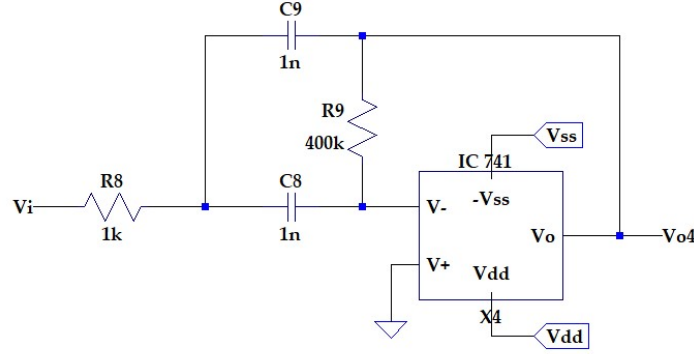


Figure 10: LTSpice schematic of multiple-feedback bandpass filter

4.3 Component Selection

The transfer function of the filter is given by

$$\frac{V_{o4}(s)}{V_i(s)} = \frac{-sC_8R_9}{s^2C_8C_9R_8R_9 + sR_8(C_8 + C_9) + 1} \quad (4)$$

Choosing $C_8 = C_9$ the filter parameters obtained are

$$H_{0BP} = -2Q^2, Q = 0.5\sqrt{\frac{R_9}{R_8}}, \omega_0 = \frac{1}{\sqrt{R_8R_9C_8}}$$

For obtaining $\omega_0 = 2\pi \times 8krad/s$, $Q = 8000/800 = 10$, the values chosen are $R_8 = 1k\Omega$, $R_9 = 400k\Omega$, $C_8 = C_9 = 1nF$.

4.4 Frequency Response

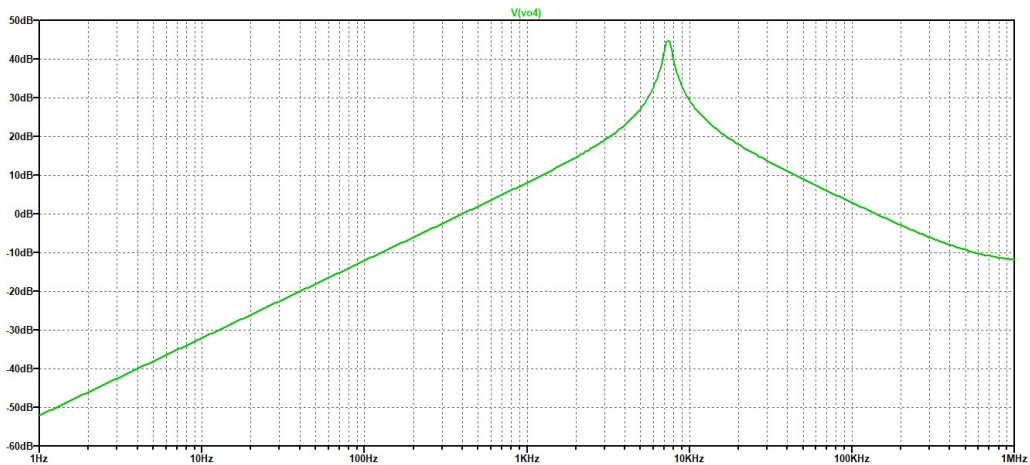


Figure 11: Frequency response of multiple-feedback bandpass filter

The figure 11 above shows the frequency response of the multiple-feedback bandpass filter. The bandwidth obtained is 603.7 Hz and the peak gain is obtained at 7.396 kHz.

4.5 Transient Response

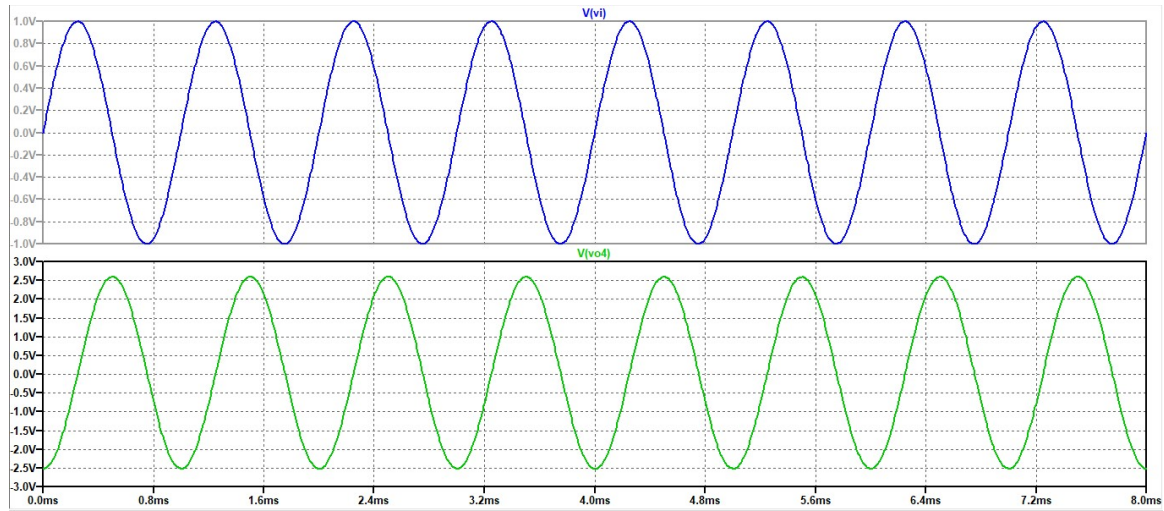


Figure 12: Transient response of multiple-feedback bandpass filter

The figure 12 above shows the transient response of the multiple-feedback bandpass filter with 1 V, 1 kHz sinewave input. The output voltage amplitude obtained is 2.56 V.

5 Conclusion

- (1). The second order active filters offer higher selectivity compared to the first order filters as they have higher stop-band attenuation.
- (2). The second order filters can be used in cascade to design higher order filters.