



INDIAN INSTITUTE OF SCIENCE, BENGALURU

DEPARTMENT OF ELECTRONIC SYSTEMS
ENGINEERING

DESIGN FOR ANALOG CIRCUITS
LABORATORY REPORT

ASSIGNMENT 8
OSCILLATORS

SOUMYA KANTA RANA
S.R. No. : 04-01-00-10-51-21-1-19261

October 9, 2021

Contents

1	Relaxation Oscillator	1
1.1	Aim	1
1.2	Schematic	1
1.3	Component Selection	1
1.4	Transient simulation waveforms	1
2	Phase Shift Oscillator	3
2.1	Aim	3
2.2	Schematic	3
2.3	Component Selection	3
2.4	Transient simulation waveforms	3
3	Three Phase Oscillator	5
3.1	Aim	5
3.2	Schematic	5
3.3	Component Selection	5
3.4	Transient simulation waveforms	5
4	Wein Bridge Oscillator	7
4.1	Aim	7
4.2	Schematic	7
4.3	Component Selection	7
4.4	Transient simulation waveforms	7
5	Conclusion	9

List of Figures

1	LTSpice schematic of Relaxation Oscillator	1
2	Transient Simulation of Relaxation Oscillator	2
3	FFT of Relaxation Oscillator output	2
4	LTSpice schematic of Phase Shift Oscillator	3
5	Transient Simulation of Phase Shift Oscillator	4
6	FFT of Phase Shift Oscillator output	4
7	LTSpice schematic of Three Phase Oscillator	5
8	Transient Simulation of Three Phase Oscillator	6
9	FFT of Three Phase Oscillator output	6
10	LTSpice schematic of Wein Bridge Oscillator	7
11	Transient Simulation of Wein Bridge Oscillator	8
12	FFT of Wein Bridge Oscillator output	8

1 Relaxation Oscillator

1.1 Aim

To design and perform transient simulation of Relaxation Oscillator.

1.2 Schematic

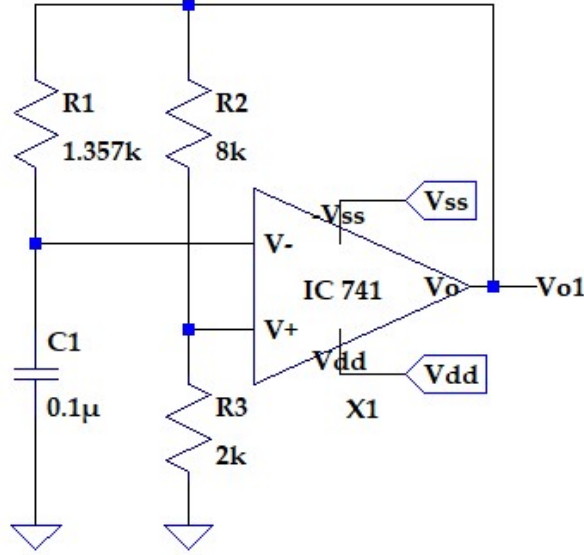


Figure 1: LTSpice schematic of Relaxation Oscillator

1.3 Component Selection

The transfer characteristics of the schmidt trigger in the circuit is given by

$$V_o = \begin{cases} -V_{sat} & , \text{ if } V_i \geq \frac{+V_{sat}R_3}{R_2+R_3} \\ +V_{sat} & , \text{ if } V_i \leq \frac{-V_{sat}R_3}{R_2+R_3} \end{cases}$$

In the simulation setup $\pm 10V$ supply is used. To set the threshold points as $\pm 2V$, $R_2 = 8k\Omega$, $R_3 = 2k\Omega$ is chosen. The time period of the oscillator in this case is given by

$$\delta t = 2R_1C_1 \ln \left(\frac{V_{sat} + 2}{V_{sat} - 2} \right)$$

For getting $f = 4545Hz$, $R_1 = 1.357k\Omega$, $C = 0.1\mu F$ is chosen.

1.4 Transient simulation waveforms

The figure 2 shows the output and the schmidt trigger input voltage waveforms, and figure 3 shows the FFT of the output voltage. The obtained frequency is 5kHz.

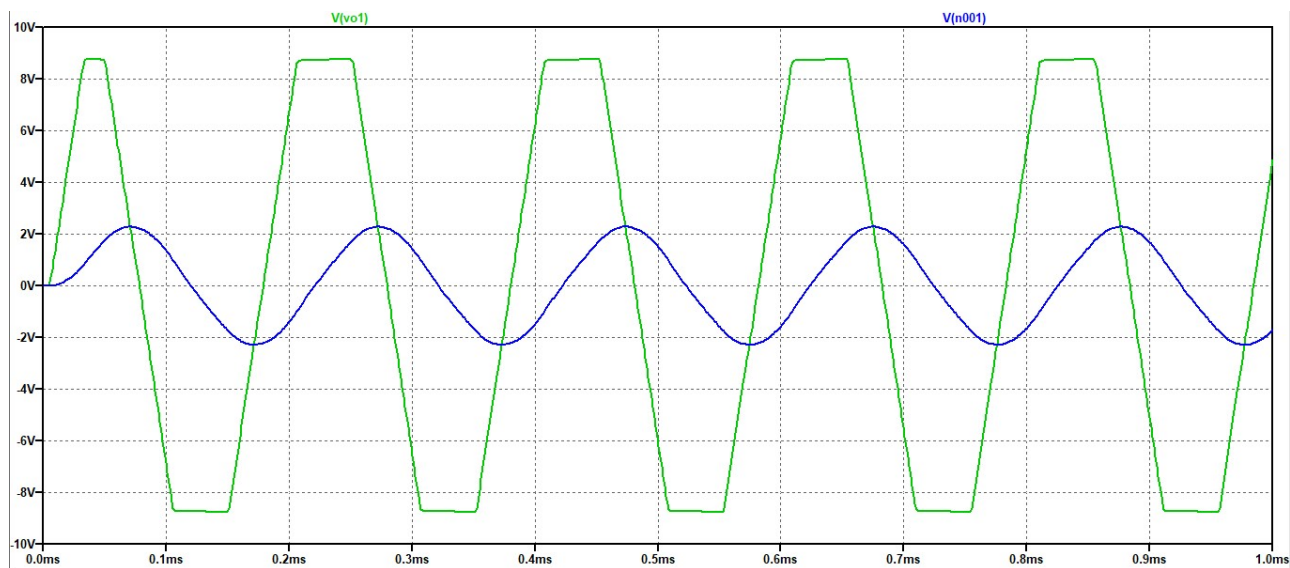


Figure 2: Transient Simulation of Relaxation Oscillator

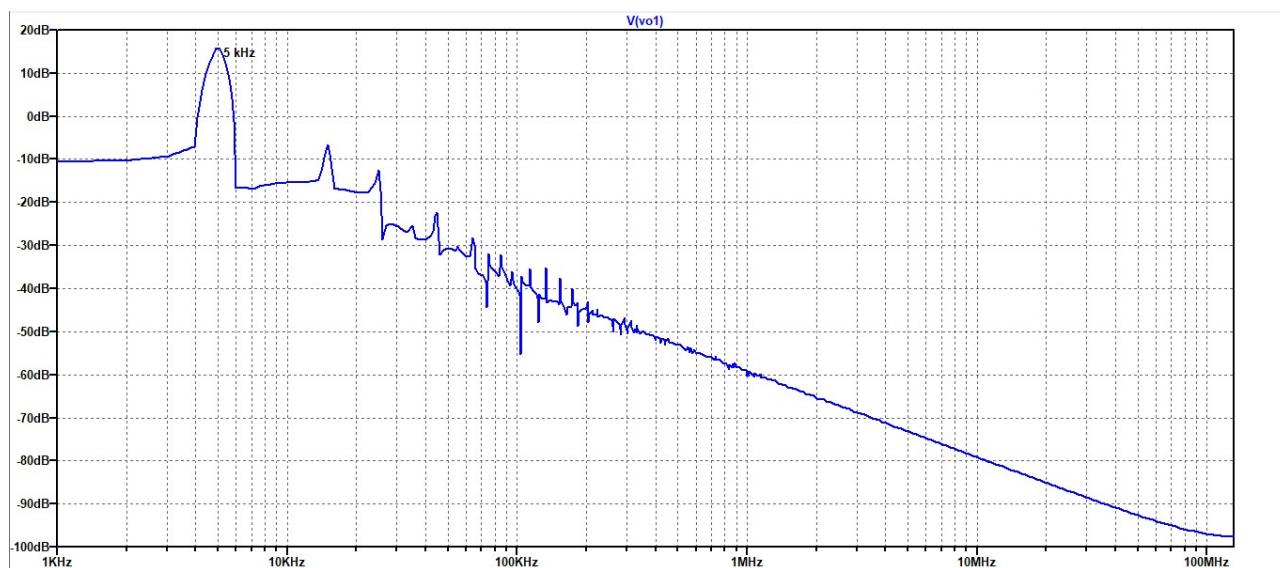


Figure 3: FFT of Relaxation Oscillator output

2 Phase Shift Oscillator

2.1 Aim

To design and perform transient simulation of Phase Shift Oscillator.

2.2 Schematic

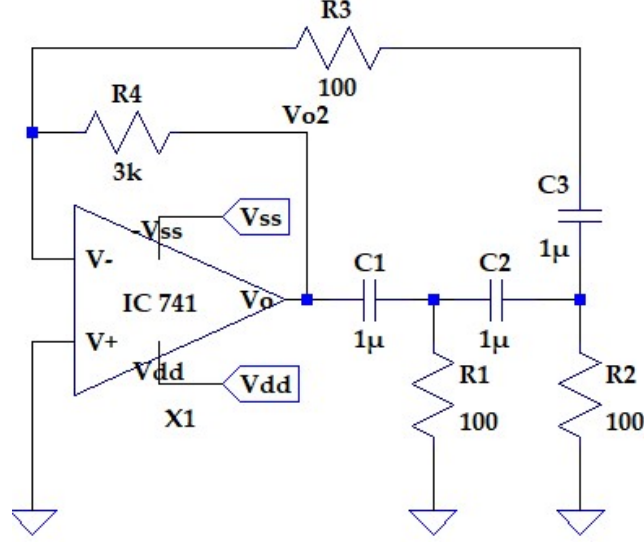


Figure 4: LTSpice schematic of Phase Shift Oscillator

2.3 Component Selection

The frequency of oscillation of the phase shift oscillator is given by

$$f = \frac{1}{2\pi\sqrt{6}RC}$$

Where $R_1 = R_2 = R_3 = R$, and $C_1 = C_2 = C_3 = C$. For obtaining a frequency of 650 Hz, $R = 100\Omega$, $C = 1\mu F$ is chosen. R_4 is chosen to be $3k\Omega$ to obtain a loop gain slightly greater than 1.

2.4 Transient simulation waveforms

Figure 5 shows the transient simulation waveforms of the phase shift oscillator after amplitude stabilisation, and figure 6 shows the FFT of the oscillator output. The oscillation frequency obtained is 632 Hz.

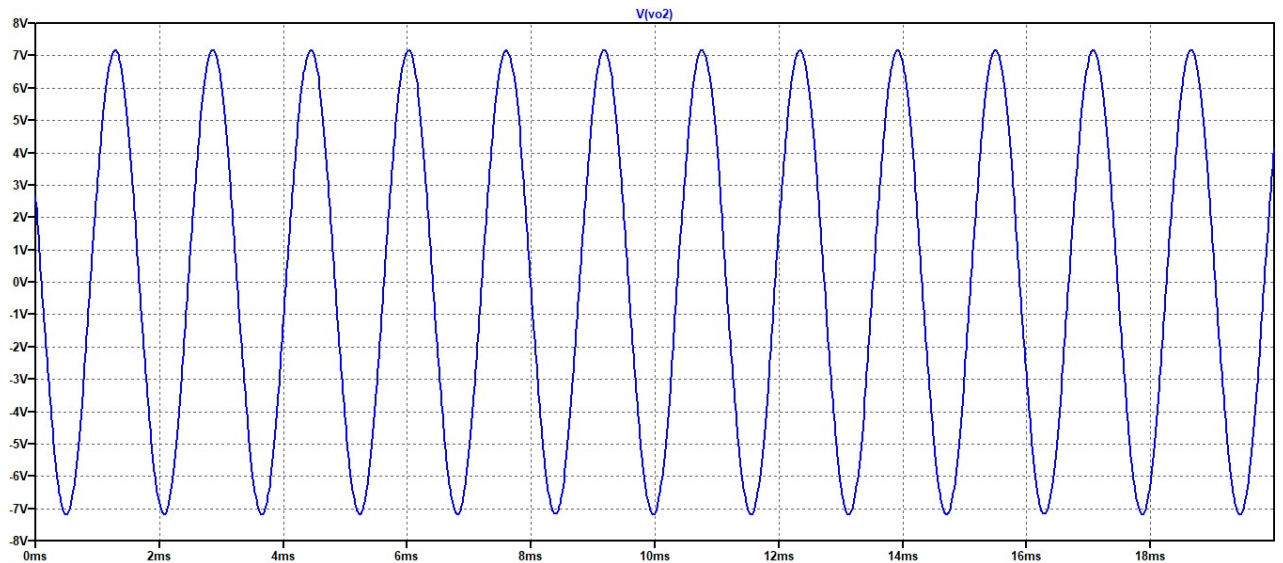


Figure 5: Transient Simulation of Phase Shift Oscillator

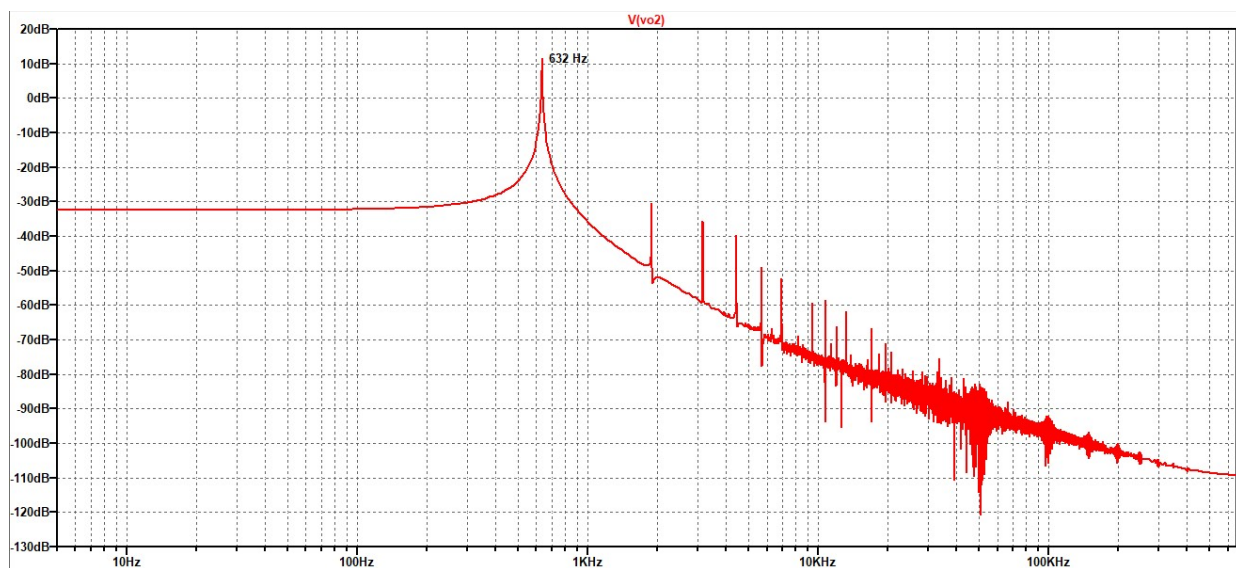


Figure 6: FFT of Phase Shift Oscillator output

3 Three Phase Oscillator

3.1 Aim

To design and perform transient simulation of Three Phase Oscillator.

3.2 Schematic

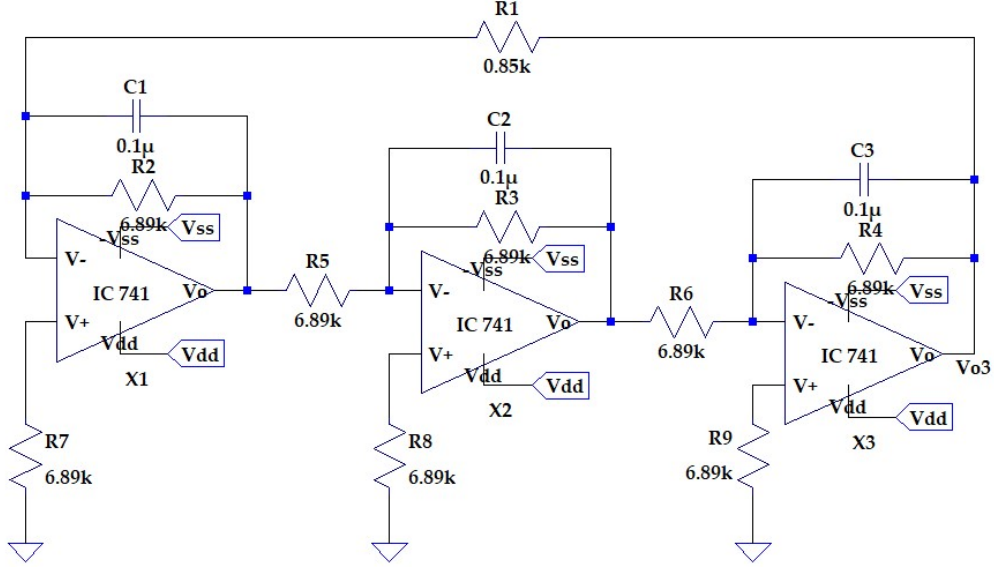


Figure 7: LTSpice schematic of Three Phase Oscillator

3.3 Component Selection

The oscillation frequency is given by

$$f = \frac{1}{2\pi\sqrt{3}RC}$$

Where $R_2 = R_3 = R_4 = R$, $C_1 = C_2 = C_3 = C$. For obtaining oscillation frequency of 400 Hz, $R = 6.89k\Omega$, $C = 0.1\mu F$ is chosen. For obtaining sustained oscillations, $R_1 = 850\Omega$ is chosen to set loop gain of 8.

3.4 Transient simulation waveforms

Figure 8 shows the transient simulation waveforms of the three phase oscillator after amplitude stabilisation , and figure 9 shows the FFT of the oscillator output. The oscillation frequency obtained is 401 Hz.

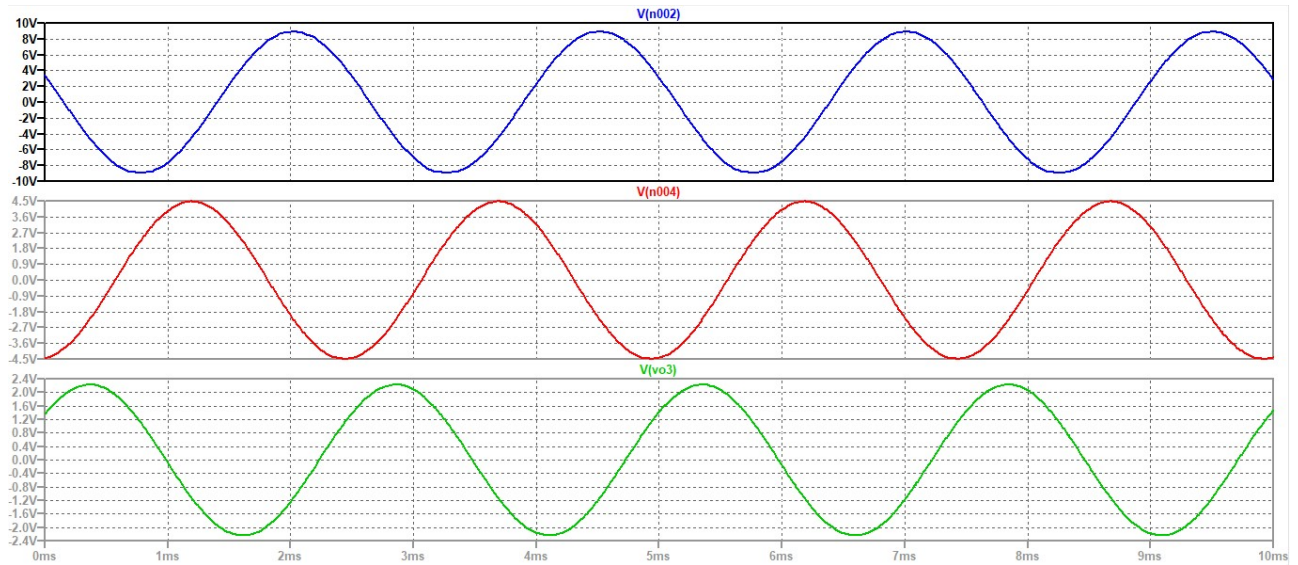


Figure 8: Transient Simulation of Three Phase Oscillator

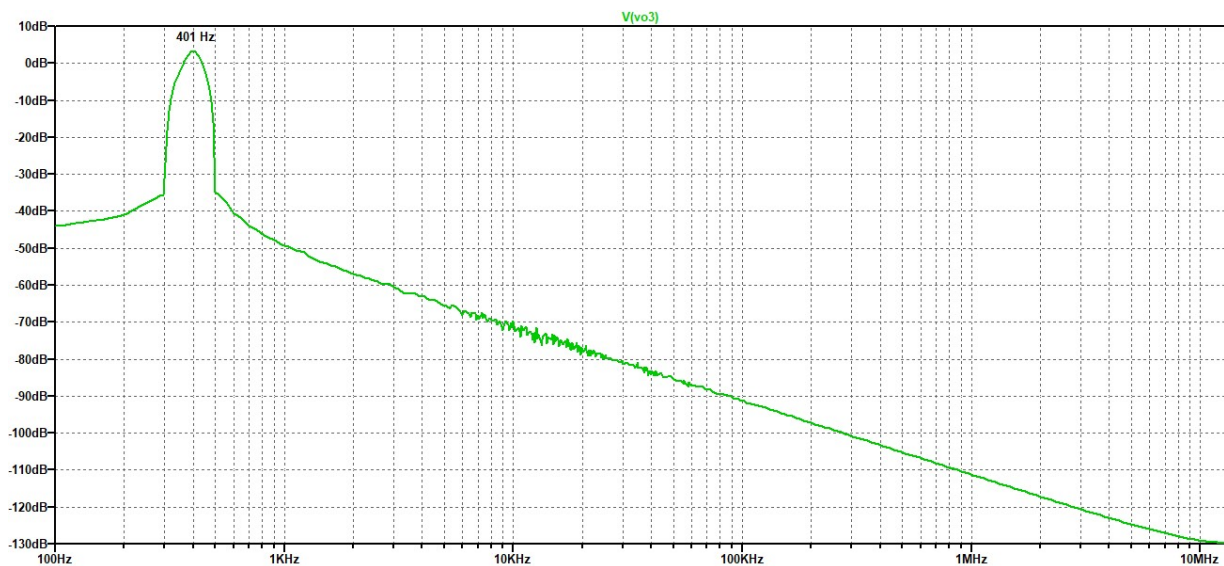


Figure 9: FFT of Three Phase Oscillator output

4 Wein Bridge Oscillator

4.1 Aim

To design and perform transient simulation of Wein Bridge Oscillator.

4.2 Schematic

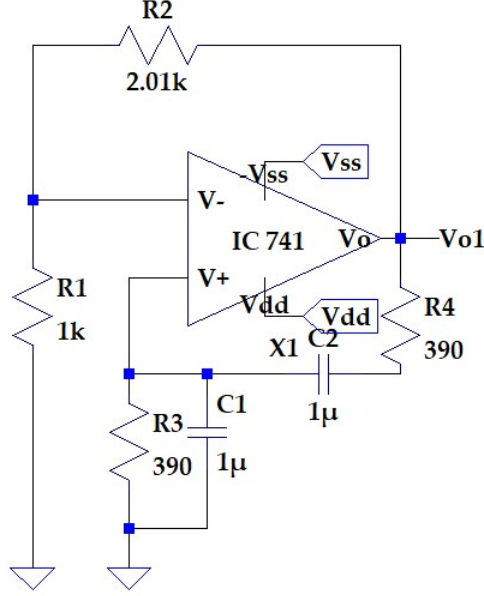


Figure 10: LTSpice schematic of Wein Bridge Oscillator

4.3 Component Selection

The frequency of oscillations is given by

$$f = \frac{1}{2\pi RC}$$

where $R_3 = R_4 = R$, $C_1 = C_2 = C$. For getting sustained oscillations $R_2/R_1 = 2$, so $R_2 = 2k\Omega$, $R_1 = 1k\Omega$ is chosen. $R = 390\Omega$, $C = 1\mu F$ is chosen for obtaining a frequency of 408 Hz.

4.4 Transient simulation waveforms

Figure 11 shows the transient simulation waveforms of the wein bridge oscillator after amplitude stabilisation, and figure 12 shows the FFT of the oscillator output. The oscillation frequency obtained is 399 Hz.

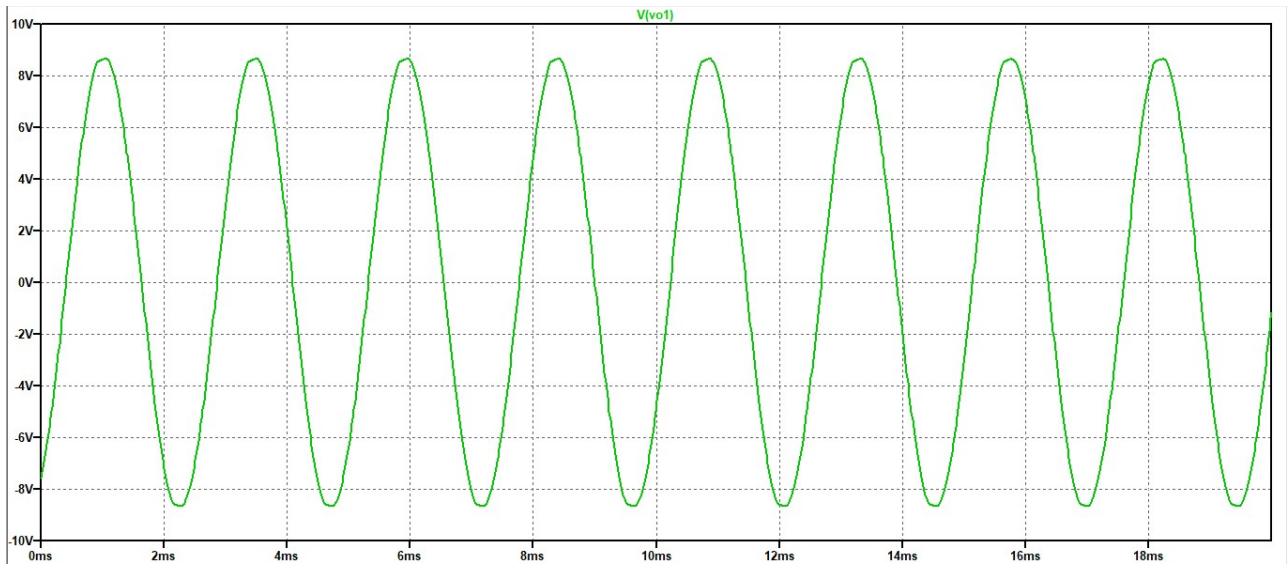


Figure 11: Transient Simulation of Wein Bridge Oscillator

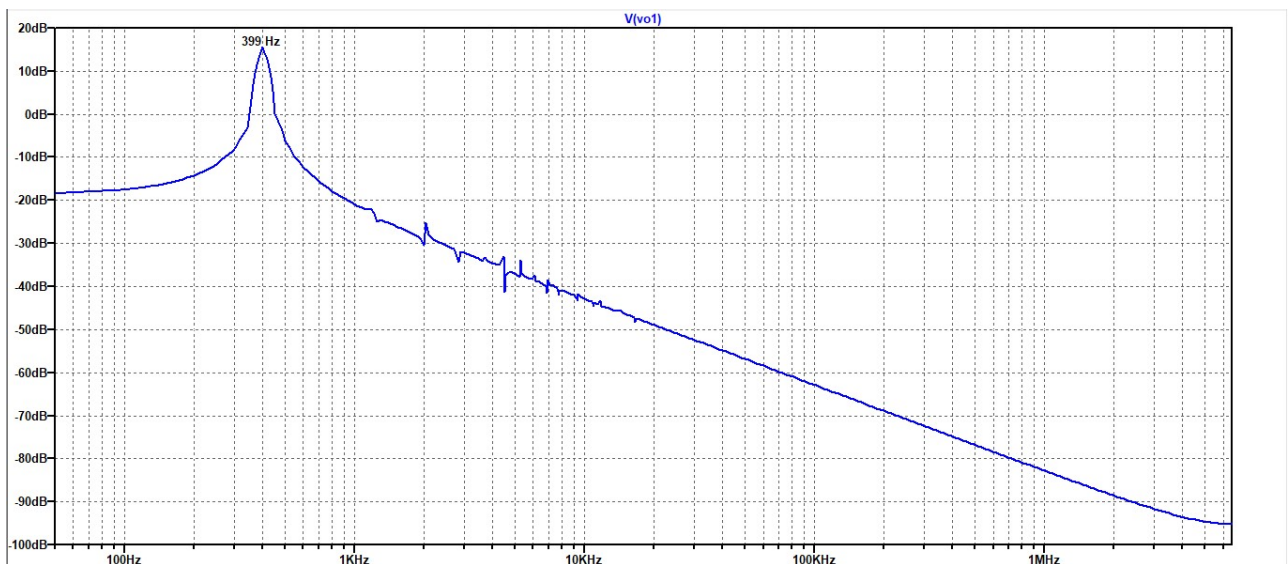


Figure 12: FFT of Wein Bridge Oscillator output

5 Conclusion

- (1). The phase shift, 3 phase and wein bridge oscillators work at the condition when barkhausen criterion is satisfied and the phase shift caused in the loop is 360° .
- (2). The oscillator being a marginally stable system, it may become unstable or it might not oscillate at slight change in component values. Tuning the frequency and obtaining stable sustained oscillations over a long period of time is a challenge.
- (3). The relaxation oscillator's frequency range is limited by the slew rate of the op-amp, as the schmidt trigger .